



Daffodil International University
Faculty of Science & Information Technology (FSIT)
Department of Software Engineering
Midterm Examination, Summer 2025
Course Code: SE 213; Course Title: Digital Electronics and Logic Design


Sections & Teachers: SP, HI, MTE, NAN, SAN SHN
Batch and Section: 43 (A to O)

Time: 1 Hour 30 Mins

Marks: 25

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

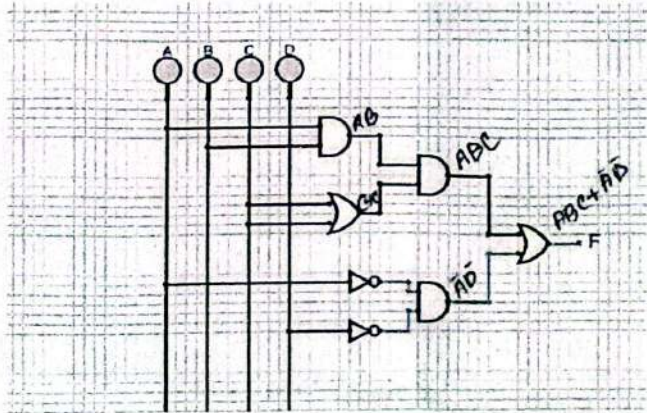1.	a)	Subtract the following using 2's complement: i) $(17)_{10} - (63)_{10}$ ii) $(101100)_2 - (1011)_2$	[Marks-3+2]	CLO-1 Level-2
	b)	Check the following circuit diagram. Express the output logic equation and simplify it: 	[Marks-5]	
2.	a)	i) Construct the Full Adder circuit using basic logic gates. ii) Apply Parallel adder to compute $(X+Y)$ along with diagram: Where $X = 1011$ and $Y = 1100$	[Marks-5+2]	CLO-2 Level-3
	b)	$F(A, B, C, D) = (A+B)(C'+D) + A \cdot C$ Apply k-map simplification technique to simplify the above expressions. Construct the logic diagrams of the simplified output.	[Marks-8]	

Digital electronics and logic design

Summer-25

Question 1%

(i) $(17)_{10} - (63)_{10}$

$\therefore 17 \rightarrow 0001001$

$63 \rightarrow 00111111$

Now:

$17 + (-63)$

$$\begin{array}{r} \Rightarrow 00010001 \\ + 11000000 \\ \hline 11010001 \end{array}$$

1's complement of 63

$\rightarrow 11000000$

$\begin{array}{r} 11000000 \\ + 1 \\ \hline 11000001 \end{array}$

\leftarrow 2's complement

Here 11010001 is negative.

as MSB = 1. To find magnitude

\rightarrow 1's complement = 00101101

\rightarrow 2's complement $\Rightarrow \begin{array}{r} 00101101 \\ + 1 \\ \hline 00101110 \end{array}$

\rightarrow result = -46

(ii) $(101100)_2 - (1011)_2$

Lets work in a 6 bit system.

101100

$001011 \rightarrow$ 1's complement $\rightarrow 110100 \rightarrow$ 2's comple. $\rightarrow 110101$

\therefore Now,

$$\begin{array}{r} 101100 \\ + 110101 \\ \hline 100001 \end{array} \Rightarrow 100001$$


Carry

MSB = 1; Negative?
Verify:

$$101100_2 = 44_{10} \rightarrow 44 - 11 = 33$$

$$001011_2 = 11_{10}$$

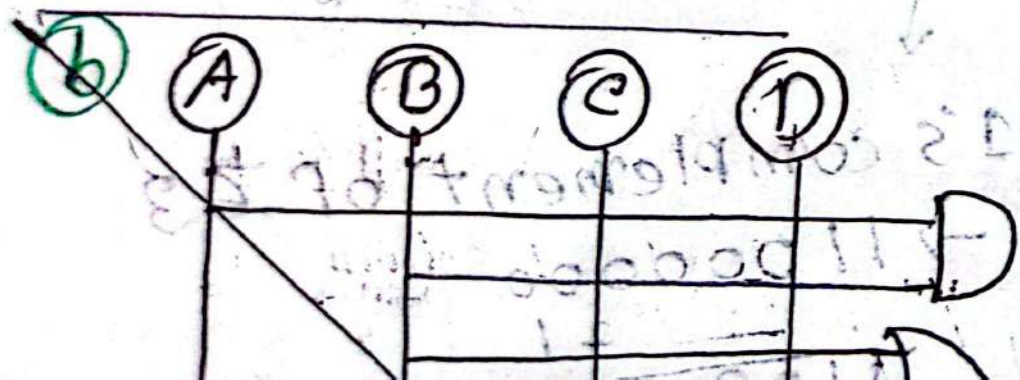
\Rightarrow So no need for 2's complementing
again as the result is Positive.



$$1001000 \leftarrow F1$$

$$1111100 \leftarrow E2$$


(b)

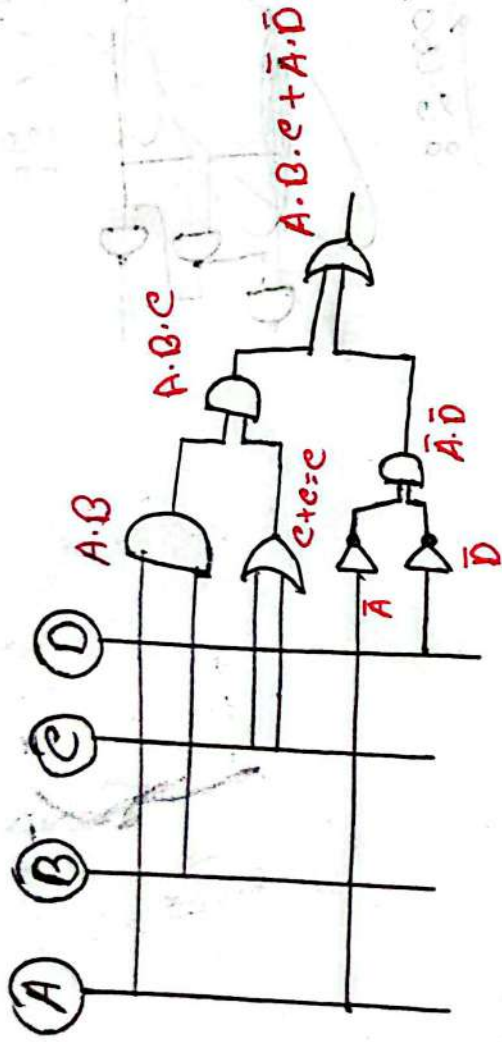

The most simplified output is $\Rightarrow ABC + \bar{A}D$

Question 20


(a)

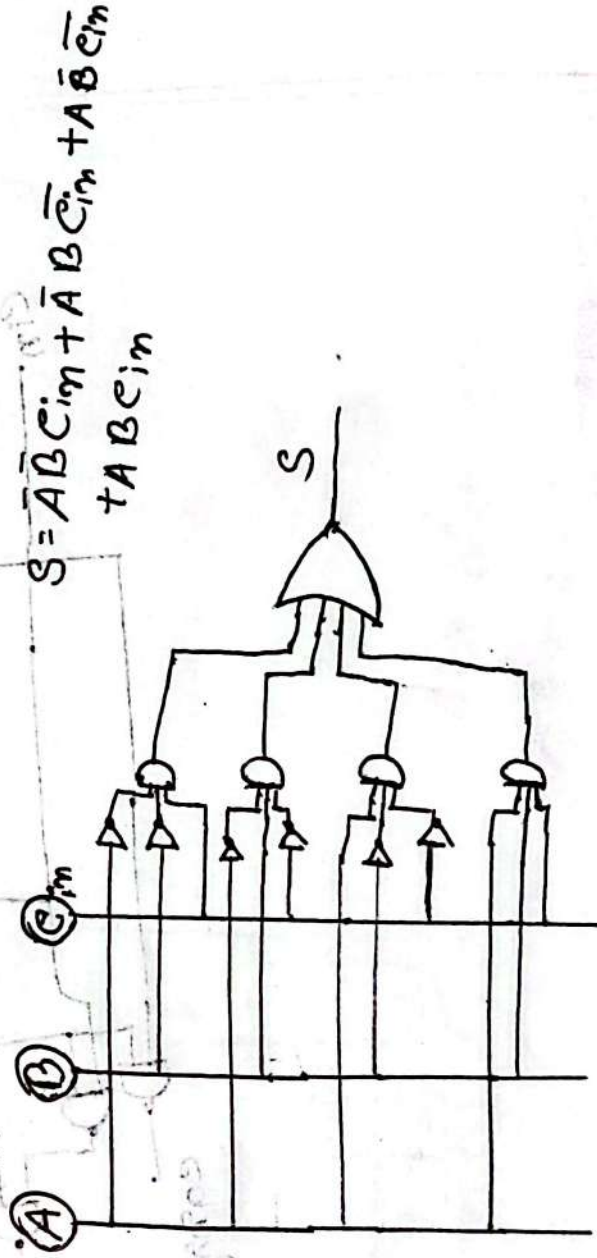


Question 28

Q

i

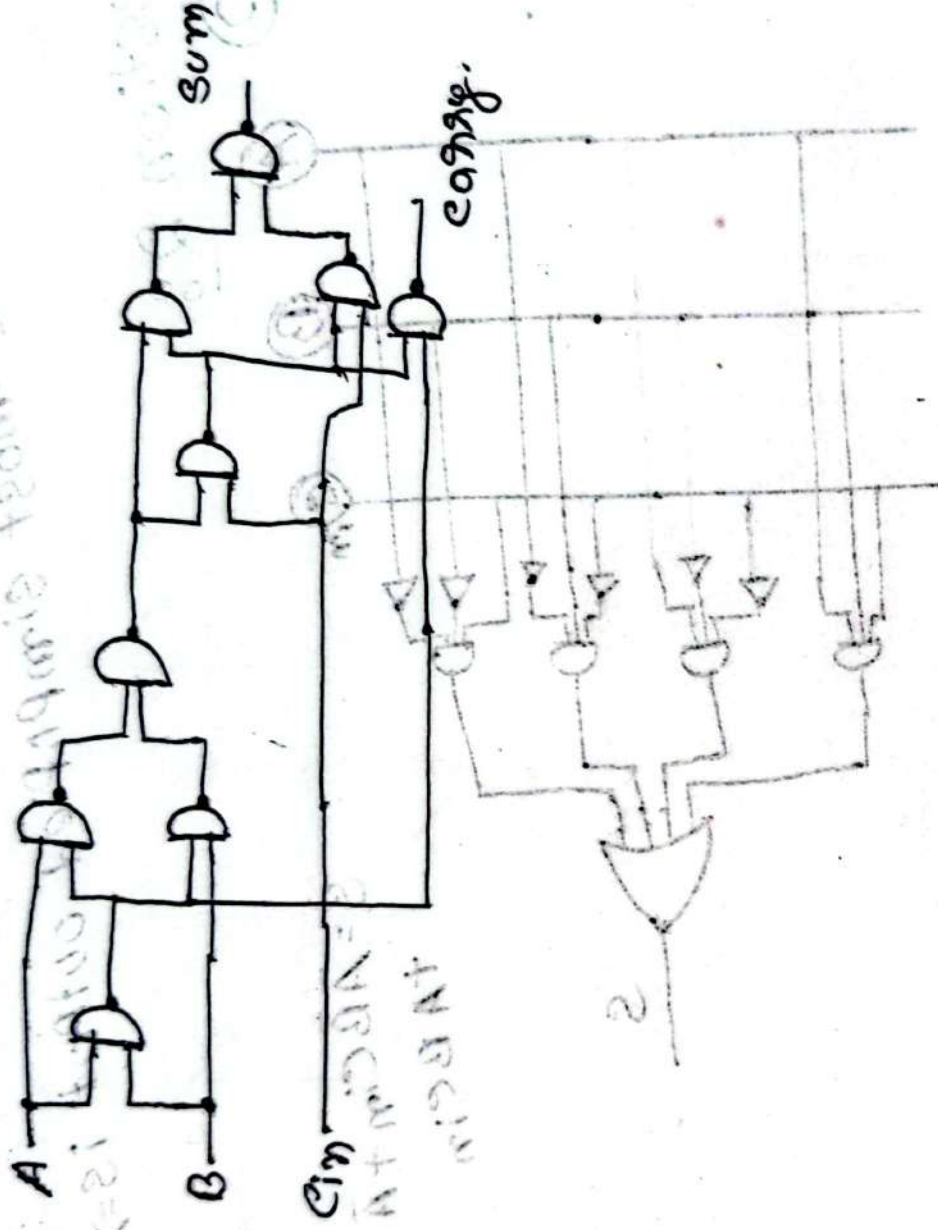

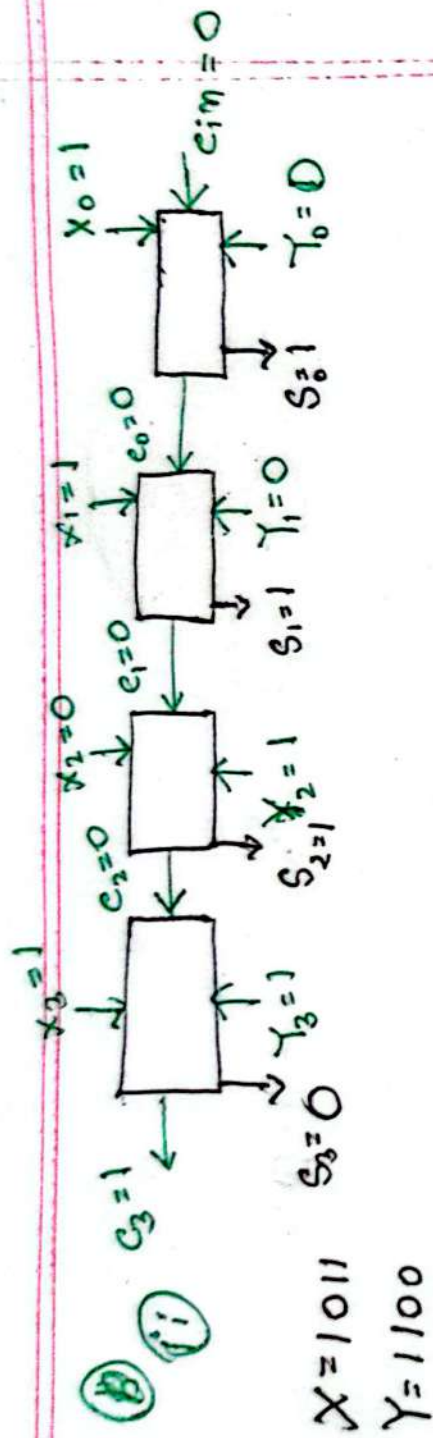

$S = 1011$
 carrying bit.

b) $F(A, B, C, D) = (A+B)(C'+D) + A \cdot C$
 $= AC' + AD + BC' + BD + AC$

min terms: (4, 5, 7, 8, 9, 10, 12, 13, 14, 15)

AB \ CD	00	01	11	10
00	0	0	0	0
01	1	1	1	0
11	1	1	1	1
10	1	1	1	1

Group 1: A
 " 2: A'B'C'
 " 3: A'B'D

$A + A'B'C' + A'B'D$

$\Rightarrow A + A'B(C' + D)$

$\Rightarrow A + B(C' + D)$

